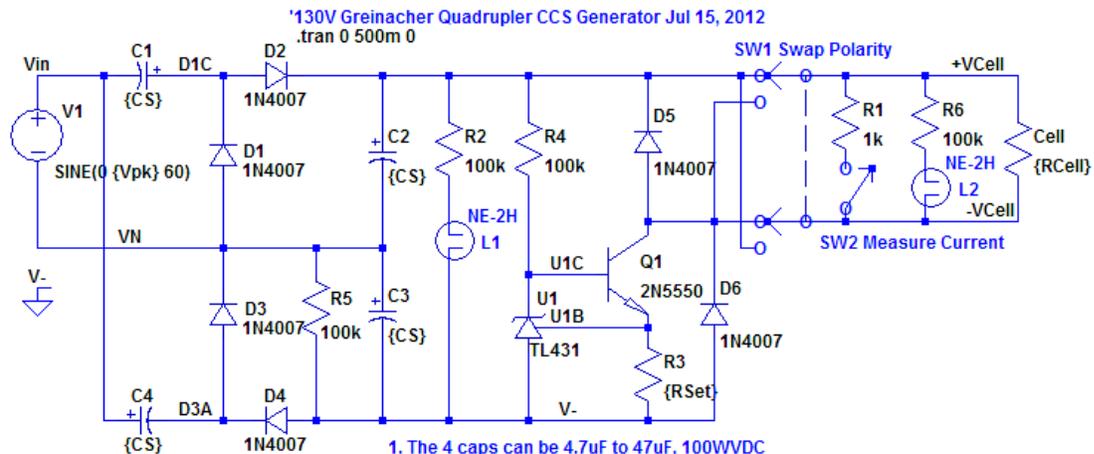


130 Volt Greinacher Quadrupler CCS Generator Jul 15 2012



```
.include tl431.sub
.param CS = 4.7uF
.param RSet = 2.5V / 0.5mA
.param Vpk = sqrt(2) * 24VXfmr
.param RCell = 150k
```

1. The 4 caps can be 4.7uF to 47uF, 100VVDC
2. Resistors are 1/4W
3. V1 is a small 24VAC transformer, \$6.99 or less on eBay.
4. SW1, DPDT, swaps polarity at the desired point in the brew
5. SW2, SPST, allows you to measure the current without having to break the connections. ($I = E / 1e3$, $0.5V = 0.5mA$)
6. Leave the circuit floating to minimize risk of shock if Q1 shorts due to ESD.
7. L2 should go out when you connect the cell. If it stays lit, then Q1 is probably shorted due to an ESD event.